FIR Filter Design

2023-fall W4823 Project Report

Tong Cao
Department of Electrical Engineering
Columbia University
New York, U.S.

Yuqi Lin Department of Electrical Engineering, Columbia University New York, U.S.

Abstract—This is a 64-tap 16-bit FIR filter.

Keywords-FIR, Verilog

I. INTRODUCTION (HEADING 1)

We know FIR computation is actually discrete convolution:


$$y[n] = \sum_{i=0}^{N} bi \cdot x[n-i].$$

x[n] is the input signal, y[n] is the output signal, N is the filter order (number of taps), bi is the filter coefficient. b and x are both 16bit fixed-point, y is 16bit half-decision floating point.

II. SIGNALS DEFINATION

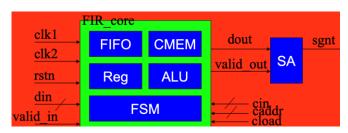A. Clock

clk1 is set as 10kHz, and the clk2 we choose is 10 times faster. Because we have asynchronous FIFO, clk2 can be set much higher than clk1.



B. Control

When rstn=0, reset the chip. cin, caddr, cload controls the process of preload, 64 coefficient (b) is loaded into CMEM consecutively following the address when cload is 1. n is input data (x) from outside, and when valid_in=1, the chip starts to compute. dout is output data (y).


III. ARCHITECTURE

Our chip is working on clk2 frequency, while input of FIFO is sent within clk1. That means the FIFO is asynchronous. First, preload b into CMEM, and pass these coefficient to on-chip register. Every very cycle, we receive a x from FIFO, grab every b store in b register, and then multiply with x, we called these product psum[i] and restore them in shift-register.


Identify applicable funding agency here. If none, delete this text box.

Every results of ALU, plus the former correspond result in shifter is the new psum[i]. Meanwhile, left-shift the psum register, and the output is connected to the psum[0] which is pushed out.

ASM:

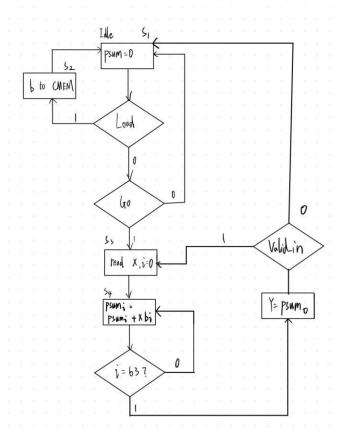

Datapath:

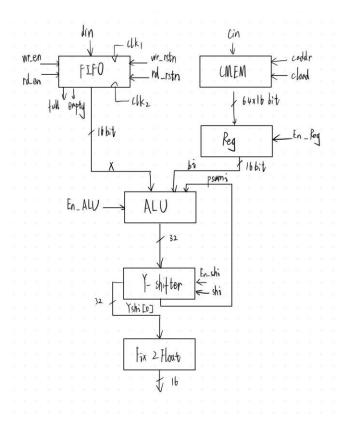

IV. BLOCKS

A. FIFO

Because of the duel FIFO clocks, we used two pointer to indicate the position of read and write operation. The FIFO's input is controlled by the clk1 and the output is controlled by the clk2, which makes it the asynchronous FIFO. The read and write are controlled by the read_ptr and write_ptr. Using the pointer to indicate the place is easy for us to insert the data or read the data. One of the beneficiaries in using pointer is that they can help us to judge if the FIFO is empty or full. The code is in fifo.v. If rd_ptr==wr_ptr, then it's empty. If wr_ptr's MSB is different with rd_ptr, while the other bits are the same, then it's full. Consider of metastable state, convert the pointer to gray code and use two stage comparison synchronizer.

B. CMEM

Generated from Memory Compiler. Sized 64x16bits. we mainly need the cmem to store the coefficients. Imem can work as the memory for the input data. In this project, we mainly use the memory compiler to generate the 64-words, 16 bits sram verilog and library file. The first problem in this project is that we need to write a RTL code (sram.v) to initialize the memory we generated using the memory compiler. Then, we write the testbench to read the coefficients file can store them in the sram array in the write mode. When writing the testbench, we need to be aware of the setup time and hold time. And then we read the data in the sram and compare them with the original data. The error stores the comparison result.

C. ALU

Our ALU has three inputs: x_local, b_local, y_former (from psum shifter), it computes x_local*b_local+y_former and send to shift register of psum.

That means, every clock cycle, we can get an output because the number of psum is different in first 64 outputs. The psum which is needed for later output is restored and fetched by ALU every cycle too.

D. FSM

We have 5 states in this design. S1 stands for idle, S2 is loading, S3 is reading coefficient from FIFO, S4 is ALU computing, S5 is shifting and output.

E. Fix to Floating Point Coverting

We finally need to generate half precision floating point result from fixpoint out of shifter. And in the testbench, the test data file we read, which is first generated by FIR definition function in Matlab and converted to fixed or floating point we need by Python code.

V. RESULTS

Startpoint: b_local_reg_2 (Fising_edge-triggered_flip-flop_clocked_by_clk2) Endpoint: adder_multipe_ALU_out_t_reg_31_ (rising_edge-triggered_flip-flop_clocked_by_clk2) Path_Group: clk2 Path_Type: max

Point	Incr	Path
clock clk2 (rise edge)	0.00	0.00
clock network delay (ideal)	0.00	0.00
b local reg 2 /CK (DFFRXLTS)	0.00 #	
b local reg 2 /QN (DFFRXLTS)	1.00	1.00 r
U6790/Y (INVX2TS)	0.20	1.19 f
U14432/Y (OAI22X1TS)	0.20	1.40 r
U14433/Y (A0I21X1TS)	0.13	1.53 f
U14434/Y (NOR2XLTS)	0.32	1.85 r
U14670/Y (A0I21X1TS)	0.20	2.05 f
U14675/S (CMPR32X2TS)	0.70	2.75 f
intadd 0 U29/C0 (CMPR32X2TS)	0.68	3.43 f
intadd_0_U28/C0 (CMPR32X2TS)	0.47	3.91 f
intadd 0 U27/CO (CMPR32X2TS)	0.47	4.38 f
intadd_0_U26/C0 (CMPR32X2TS)	0.47	4.85 f
intadd_0_U25/C0 (CMPR32X2TS)	0.47	5.33 f
intadd_0_U24/C0 (CMPR32X2TS)	0.47	5.80 f
intadd_0_U23/C0 (CMPR32X2TS)	0.47	6.27 f
intadd_0_U22/C0 (CMPR32X2TS)	0.47	6.75 f
intadd_0_U21/C0 (CMPR32X2TS)	0.47	7.22 f
intadd_0_U20/C0 (CMPR32X2TS)	0.47	7.69 f
intadd_0_U19/C0 (CMPR32X2TS)	0.47	8.16 f
intadd_0_U18/C0 (CMPR32X2TS)	0.47	8.64 f
intadd_0_U17/C0 (CMPR32X2TS)	0.47	9.11 f
intadd_0_U16/C0 (CMPR32X2TS)	0.47	9.58 f
intadd_0_U15/C0 (CMPR32X2TS)	0.47	10.06 f
intadd_0_U14/C0 (CMPR32X2TS)	0.47	10.53 f
intadd_0_U13/C0 (CMPR32X2TS)	0.47	11.00 f
intadd_0_U12/CO (CMPR32X2TS)	0.47	11.48 f
intadd_0_U11/CO (CMPR32X2TS)	0.47	11.95 f
intadd_0_U10/C0 (CMPR32X2TS)	0.47	12.42 f
intadd_0_U9/C0 (CMPR32X2TS)	0.47	12.89 f
intadd_0_U8/C0 (CMPR32X2TS)	0.47	13.36 f
intadd_0_U7/C0 (CMPR32X2TS)	0.47	13.84 f
intadd_0_U6/C0 (CMPR32X2TS)	0.47	14.31 f
intadd_0_U5/C0 (CMPR32X2TS)	0.47	14.78 f
intadd_0_U4/C0 (CMPR32X2TS)	0.47	15.26 f
intadd_0_U3/C0 (CMPR32X2TS)	0.47 0.46	15.73 f 16.19 f
intadd_0_U2/C0 (CMPR32X2TS) U14834/Y (XOR2XLTS)	0.46	16.19 f
	0.21	16.40 f
adder_multipe_ALU_out_t_reg_31_/D (EDFFX1TS) data_arrival_time	0.00	16.40
data arrivat time		10.40
clock clk2 (rise edge)	1000.00	1000.00
clock network delay (ideal)	0.00	1000.00
adder multipe ALU out t req 31 /CK (EDFFX1TS)	0.00	1000.00 r
library setup time	-0.77	999.23
data required time	-0.77	999.23
data required time		
data required time		999.23
data arrival time		-16.40
data diritat time		-10.40
slack (MET)		982.83

